

---

# ELEC 4700 Assignment 4

## Table of Contents

Question 1 and 2 .....	1
Question 3 .....	6
Question 4 - Transient Circuit Analysis .....	10
Q4d - Step Response .....	12
Q4d - Step Response increasing time step .....	14
Q4d - Sine wave @ Different frequency .....	16
Q4d - Sine wave @ Different frequency increasing time step .....	21
Q4d - Gaussian Pulse Response .....	23
Question 5 - Introduction of circuit noise .....	25
Q5 Changing Cn .....	29
Q5 Changing Time Step .....	34

Circuit Modeling - Jinseng Vanderkloot 101031534 - Due: April 10, 2022

## Question 1 and 2

%Modify Assignment 3 Questions 2 to calculate the resistance for variable  
%This will sweep the bottleneck area from 0.1V to 10V to calculate the  
%resistance in the area and apply a linear fit to the IV curve

```
%Initial
m0 = 9.10938215e-31;           % electron mass
mn = 0.26*m0;                  % Effective mass
Temp = 300;                     % Initial Temp (K)
kb = 1.3806504e-23;            % Boltzmann constant
tmn = 0.2e-12;                 % Mean time between collision
q = 1.602e-19;                 % Charge of an Electron (Assignment 3 for
    force)

% Region Area
wArea = 200e-9;
lArea = 100e-9;

%Thermal Velocity (Question 1.A)
vt=sqrt((2*kb*Temp)/mn);       % Sim in 2D so (2*kb*Temp), 3D is (3*kb*Temp)

%Electron motion
numElec = 1000;                %Number of simulated Electrons.
numEPlot = 30;                 %Number of plotted Electrons
dt = (lArea*wArea)/2;          %Typically 1/100 of region size
stepsTot = 200;                %Total amount of steps (1000 was a long
    simulation)
tTot= stepsTot*dt;              %Total Simulation time
x = zeros(1,numElec);           %Initial X matrix
y = zeros(1,numElec);           %Initial y matrix
vx = zeros(1,numElec);          %Initial velocity x matrix
```

```
vy = zeros(1,numElec);           %Initial velocity y matrix
vtot = zeros(1,numElec);         %Initial velocity matrix
xfield = zeros(1,numElec);       %Initial Position in E field x
yfield = zeros(1,numElec);       %Initial Position in E field y
vxForce = zeros(1,numElec);      %Initial Force due to position in E field x
vyForce = zeros(1,numElec);      %Initial Force due to position in E field y

%Probability of Scatter
scatOn = 1;                       %Turn Scatter on (1) or off(0)
Pscatter = 1-exp(-dt/tmn);        %Scatter Equation
tScatter = zeros(1,numElec);

%Bottle Neck Boundary reduced to prevent bleeding
% X limit (no particle between X1 and X2 - Cosider Y limits)
boxX1=80e-9;
boxX2=120e-9;
% Y Limit (no particles between 0 and Y1 and Y2 to Y limit)
boxY1 = 40e-9;
boxY2 = 60e-9;

%Electric Field
x0 = 0.5; %voltage at right side of area increased to 0.5V to see huge effect
x1 = 0; %Voltage at left side of area
nx = wArea*1e9; % # of colums (changes to have same ratio as A1 area 2/1)
ny = lArea*1e9; % # of rows
xBox = 40; %Width of box (changes to same box ratio as A1 area l= 40 and w=40)
yBox = 40; %Hight of box
boxCond = 0.01;

%Electron Graph
for cnt = 1:numElec
    x(cnt)=rand()*wArea;
    y(cnt)=rand()*lArea;
    %If the electrons are place in the box, re-roll position
    while (x(cnt)>=boxX1 && x(cnt)<=boxX2 && (y(cnt)<=boxY1 ||
y(cnt)>=boxY2))) %Relocate them if in boundary
        x(cnt)=rand()*wArea;
        y(cnt)=rand()*lArea;
    end
    vx(cnt)=(vt/sqrt(2))*randn(); % velocity * Gaussian dist
    vy(cnt)=(vt/sqrt(2))*randn(); % velocity * Gaussian dist
    vtot(cnt)= sqrt (vx(cnt)^2)+(vy(cnt)^2);
    colors= rand(numElec,3);
end

%Boundary Energy/Velocity loss coefficient (reduction in velocity =
%reduction in temprature)
vloss = 0.95;

vol = 0.1 : 0.5 : 10.1; %Sweep the device from 0.1V to 10V
vStep = 1;

% Main Loop
for voltage = vol
```

---

```
V=A2_Function(nx, ny, xBox, yBox, boxCond, voltage, x1);
Vmap = reshape(V, [ny, nx]);
[Ex,Ey] = gradient(-Vmap);
t=0;
intCNT = 2;
while t < tTot
    t = t + dt;

    %Store old position
    oldx = x;
    oldy = y;

    %Update to new position
    x(1:numElec) = x(1:numElec) + (vx(1:numElec).*dt);
    y(1:numElec) = y(1:numElec) + (vy(1:numElec).*dt);

    vtot(1:numElec)= sqrt ((vx(1:numElec).^2)+(vy(1:numElec).^2));

    for check = 1:numElec
        %Scatter
        if scatOn==1
            if Pscatter > rand()
                vx(check)=(vt/sqrt(2))*randn();
                vy(check)=(vt/sqrt(2))*randn();
                tScatter(check)= 0; %If collision, time goes to 0
            else
                tScatter(check)= tScatter(check) + dt; %track time
            end
        end
        increaing while no collision
        end

        % Bring X and Y of particle location to values able to be tracked
        % in electric field mesh to apply field forces
        xfield(check) = round(x(check)*1e9);
        yfield(check) = round(y(check)*1e9);

        %Make sure field effects still apply to particles which go across
        %area
        if xfield(check)>200
            xfield(check) = 200;
        end
        if xfield(check)<1
            xfield(check) = 1;
        end
        if yfield(check)>100
            yfield(check) = 100;
        end
        if yfield(check)<1
            yfield(check) = 1;
        end
        %Apply field force to particles
        vxForce(check)= ((q *Ex(yfield(check),xfield(check)))/(wArea/nx))/
mn)*dt; % V=(q*E)/mass F=q*E
```

---

```

        vyForce(check)= ((q *Ey(yfield(check),xfield(check)))/(lArea/ny))/
mn)*dt; % V=(q*E)/mass F=q*E
        vx(check) = vx(check)+ vxForce(check);
        vy(check) = vy(check)+ vyForce(check);

        %Apply Boundary Conditions
        %If bottom contact, bounce off in opposite direction
        if (y(check)<=0)
            y(check) = 0;
            vy(check) = -vy(check);
        end
        %If top contact, bounce off in opposite direction
        if (y(check)>=lArea)
            y(check) = lArea;
            vy(check) = -vy(check);
        end
        %If left side of box, come out right side
        if(x(check)<=0)
            x(check) = x(check) + wArea;
        end
        %If right side of box, come out left side
        if(x(check)>=wArea)
            x(check) = x(check) - wArea;
        end

        %Apply bottle neck conditions
        %If contact on left walls of boundary (not in Gap)
        if (oldx(check)<boxX1 && x(check)>=boxX1 && (y(check)<= boxY1 ||
y(check)>= boxY2) && oldx(check)>((1/5)*wArea) && oldx(check)<((4/5)*wArea))
            x(check)=boxX1;
            vx(check) = -(vx(check)*vloss);
        end
        %If contact on right walls of boundary (not in Gap)
        if (oldx(check)>boxX2 && x(check)<=boxX2 && (y(check)<= boxY1 ||
y(check)>= boxY2) && oldx(check)>((1/5)*wArea)&& oldx(check)<((4/5)*wArea))
            x(check)=boxX2;
            vx(check) = -(vx(check)*vloss);
        end
        %If contact with bottom boundary in gap
        if (x(check)>boxX1 && x(check)< boxX2 && oldy(check)>boxY1 &&
y(check)<= boxY1)
            y(check)= boxY1;
            vy(check) = -(vy(check)*vloss);
        end
        %If contact with top boundary in gap
        if (x(check)>boxX1 && x(check)< boxX2 && oldy(check)<boxY2 &&
y(check)>=boxY2)
            y(check)=boxY2;
            vy(check) = -(vy(check)*vloss);
        end
    end

    %Current over time with Field - Mistake multiplying current by L and W
    %- Only multiply with W cause density is A/m * m

```

---


```

Ix(:,intCNT)= q*10e19*mean(vx)* wArea; %Current = e * n * vd * Area
(Particle density)

intCNT = intCNT +1;
end
AvgIx (:,vStep) = mean (Ix);
vStep = vStep +1;
end
figure(1); hold on;
p = polyfit(vol,AvgIx,1);
line = polyval(p,vol);
plot(vol,AvgIx,"r");
plot(vol,line,'b');
title('Current in Area for Changing voltage'),xlabel('Voltage(V)', 'FontSize',
10), ylabel('Current(A)', 'FontSize', 10);
legend ('Current', 'Linear Fit');
fprintf('Linear equation is I = %e * V + %e \r', p(1), p(2));
R3 = 1/(p(1));
fprintf('The resistance for R3 = %e Ohms \r',R3);
hold on;

```

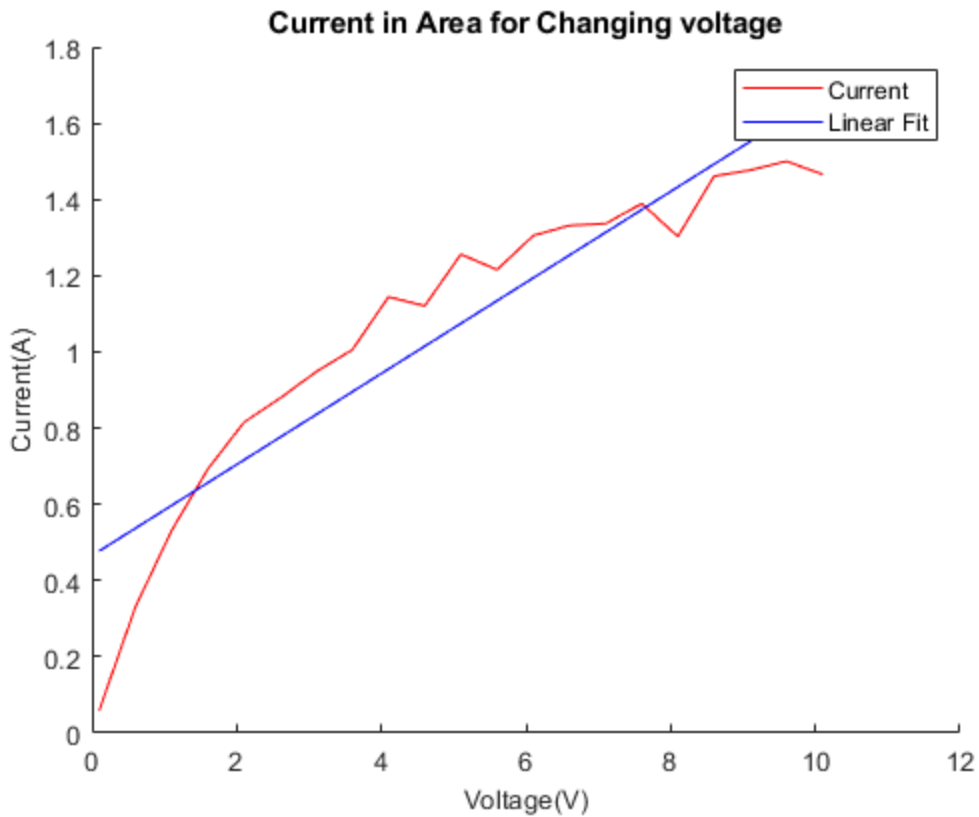Linear equation is  $I = 1.194209e-01 * V + 4.654612e-01$  The resistance for  $R3$   
 $= 8.373740e+00$  Ohms



## Question 3

```
%This is PA7 with DC and AC sweep of circuit for A4

% The Differential Equations for the circuit are the following:

% 0 = Iin - G1(V1-V2) - C*d(V1-V2)/dt
% 0 = G1(V1-V2) + C*d(V1-V2)/dt - V2*G2 - IL
% 0 = IL - G3*V3
% 0 = I4 - G4*(V4-V5)
% 0 = G4*(V4-V5) - Go*Vo
% Vin = V1
% V4 = I3*Alpha = -Alpha*G3*V3
% dIL = dt(V2-V3)/L

% 1B Frequency Domain
    %Values to put into matrix

% 0 = Iin - G1(V2-V1) - jwC*(V2-V1)
    % V1*(-G1)    Iin    V2*(G1)
% 0 = G1(V2-V1) + jwC*(V2-V1) - V2*G2 - IL
    % V1(G1)    V2(-G1 + -G2)    -IL
% 0 = IL - G3*V3
    % IL    V3(-G3)
% 0 = I4 - G4*(V4-V5)
    % I4    V4(-G4)    V5 (G4)
% 0 = G4*(V4-V5) - Go*V5
    %V4(G4)    V5 (-G4-G0)
% Vin = V1
    %Vin(t)    V1
% V4 = I3*Alpha = -Alpha*G3*V3
    %V4    V3 (-Alpha*G3)
% IL = (1/jwL)*(V2-V3)
    %1/L    V2    -V3

C=0.25;
G1 = 1;
G2 = 1/2;
G3 = 1/8.5;
G4 = 1/0.1;
G0 = 1/1000;
L = 0.2;
alpha = 100;

%F = V1, V2, V3, V4, V5, Vin, I4, IL

CVec = [-C, C, 0, 0, 0, 0, 0, 0;
        C, -C, 0, 0, 0, 0, 0, 0;
        0, 0, 0, 0, 0, 0, 0, 0;
        0, 0, 0, 0, 0, 0, 0, 0;
        0, 0, 0, 0, 0, 0, 0, 0;
        0, 0, 0, 0, 0, 0, 0, 0;
        0, 0, 0, 0, 0, 0, 0, 0;
```

```
0, 0, 0, 0, 0, 0, 0, 0, 0;
0, 0, 0, 0, 0, 0, 0, 0, -L;]; %Not 1/L

GVec = [-G1, G1, 0, 0, 0, -1, 0, 0, 0;
        G1, -G1-G2, 0, 0, 0, 0, 0, 0, -1;
        0, 0, -G3, 0, 0, 0, 0, 0, 1;
        0, 0, 0, -G4, G4, 0, 1, 0, 0;
        0, 0, 0, G4, -G4-G0, 0, 0, 0, 0;
        1, 0, 0, 0, 0, 0, 0, 0, 0;
        0, 0, -alpha*G3, 1, 0, 0, 0, 0, 0;
        0, 1, -1, 0, 0, 0, 0, 0, 0;];

FVec = [0;0;0;0;0;0;1;0;0];

%DC Sweep
vin = linspace(-10,10);
threeV = zeros(size(vin));
outputV = zeros(size(vin));
for a = 1:size(vin,2)
    V = (GVec+CVec)\(FVec.*vin(a));
    threeV(a) = V(3);
    outputV(a) = V(5);
end

figure('name','DC Sweep')
plot(vin,threeV,'g');
hold on
plot(vin,outputV,'r');
hold off
title('DC Sweep');
xlabel('Input Voltage (V)');
ylabel('Output Voltage (V)');
legend('V3','Vout');

% AC Sweep
freq = linspace(0.01, 100);
threeV = zeros(size(vin));
outputV = zeros(size(freq));
for a = 1:size(freq,2)
    w = (2*pi*freq(a));
    jw = 1i*w; % 1i makes value complex 1 -> 0+1j
    V = (GVec+jw*CVec)\FVec;
    outputV(a) = V(5);
    threeV(a) = V(3);
end

figure('Name','AC Sweep')
plot(2*pi*freq,real(outputV),'g'); %Real() gets rid of imag value warning
xlim([0 100])
hold on
plot(2*pi*freq,real(threeV),'r');
hold off
title('AC Sweep')
xlabel('Frequency (Hz)')
```

```


ylabel('Output (V)')
legend('Vout', 'V3');

%Capacitor normal Distribution
C = 0.25 + 0.05 * randn(1000,1); %Random C values
outputV = zeros(size(C));
for a = 1:size(C,1)
    CVec(1:2,1:2)=C(a); %CVec does not auto update for changing C so need this
    statement
    V = (GVec+(1i*pi)*CVec)\FVec;
    outputV(a) = V(5);
end



figure('Name','Capacitor Distribution')
histogram(C);
title('Capacitor Distribution');
xlabel('Capacitance (F)');
ylabel('Number (#)');


figure('Name','Output Distribution');
histogram(real(outputV));
title('Output Distribution');
xlabel('Vout (V)');
ylabel('Number (#)');

```

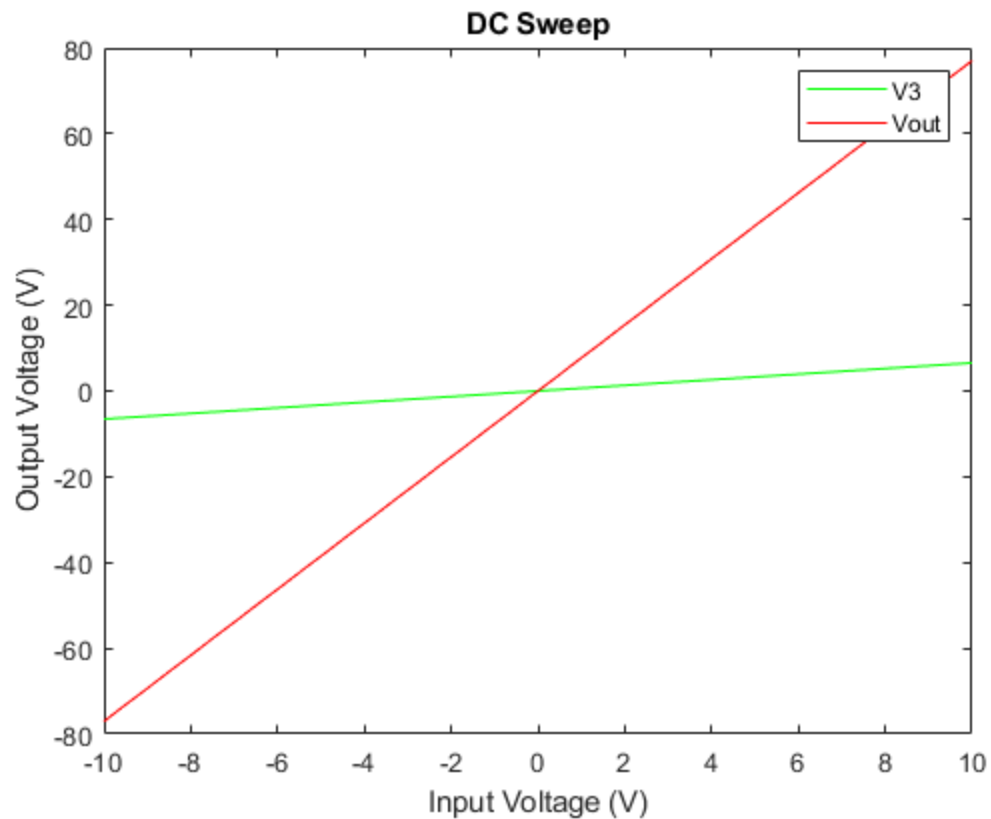



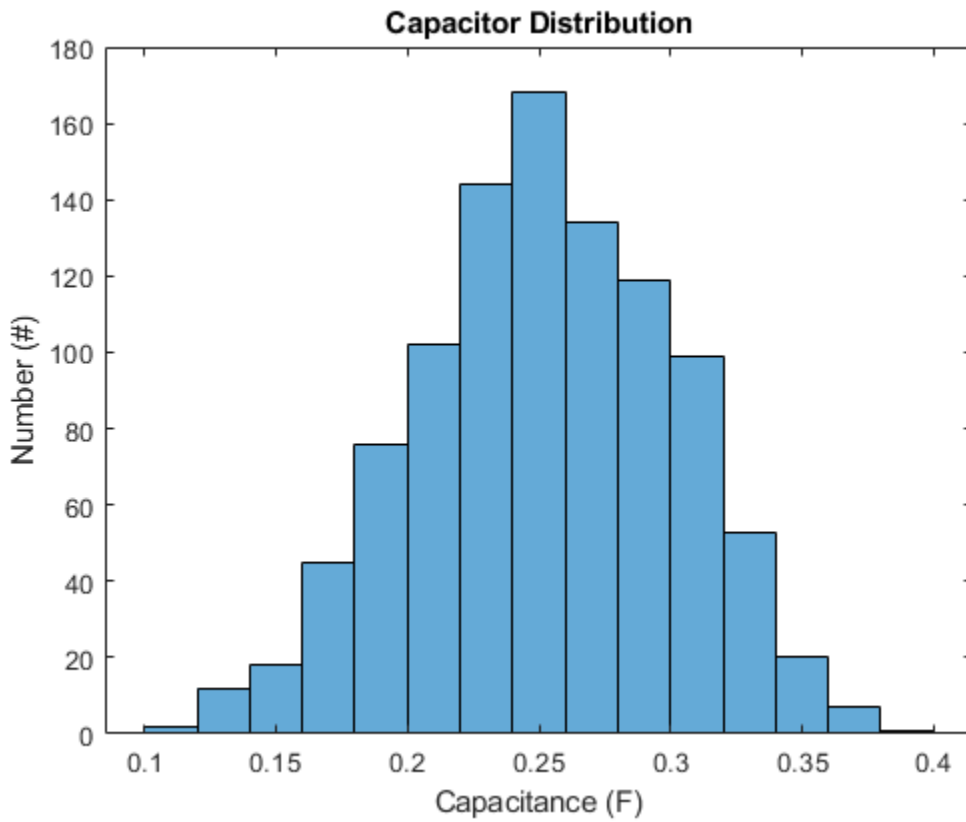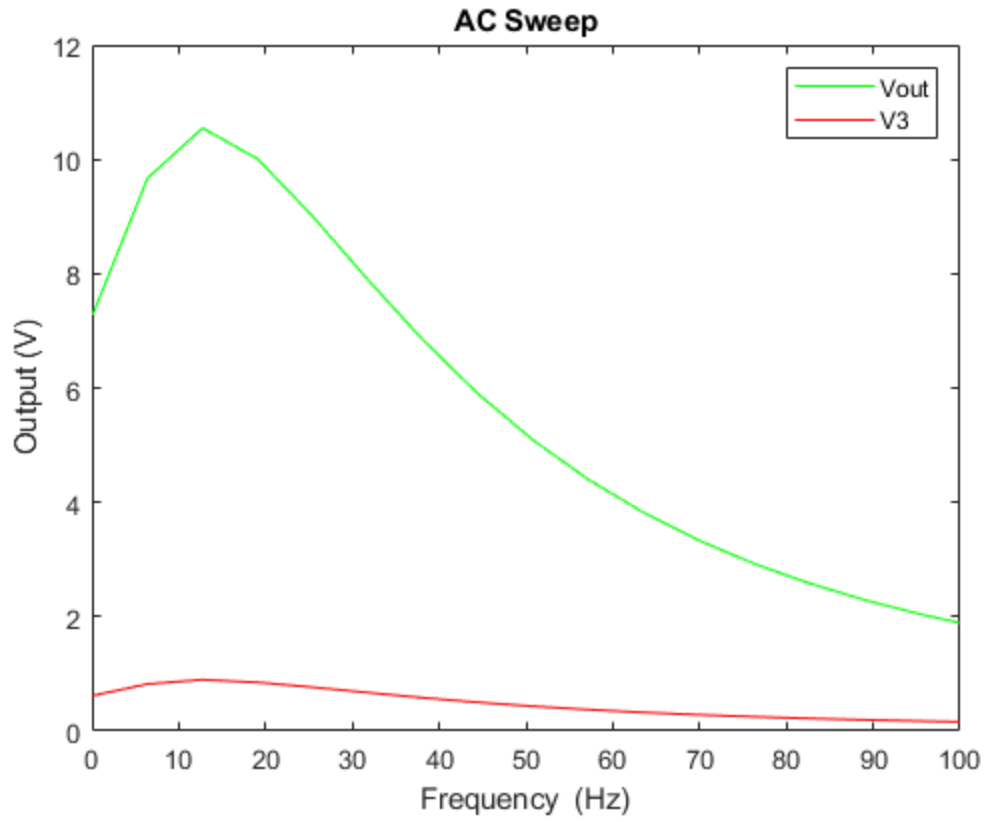

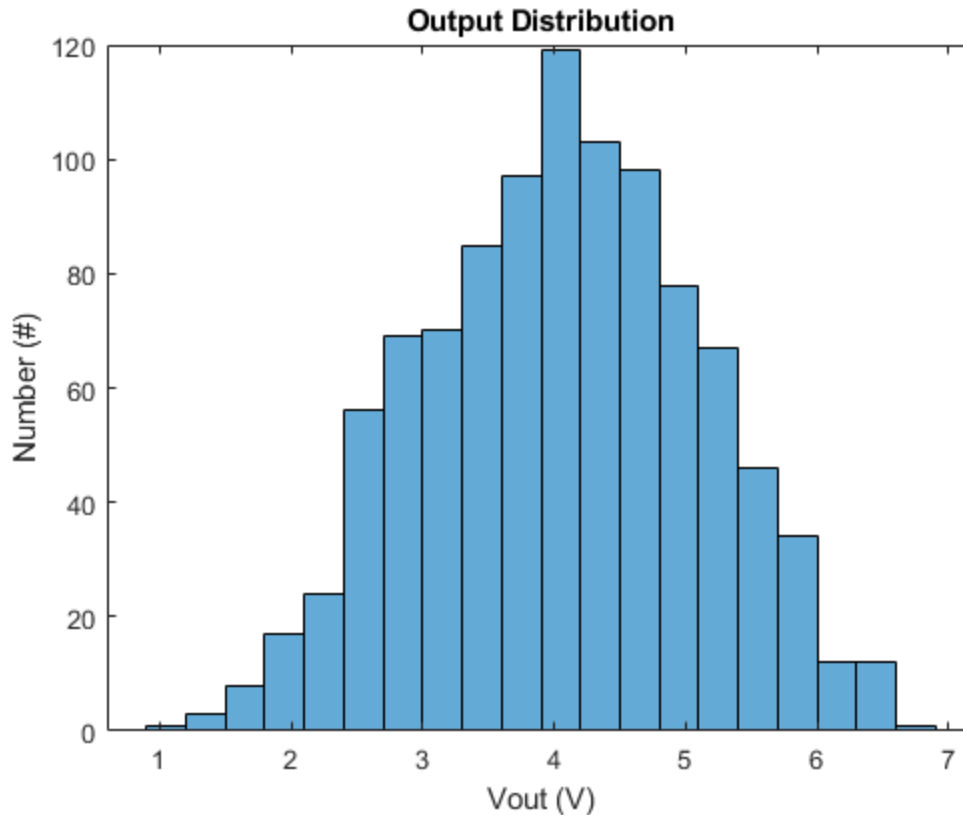

## Question 4 - Transient Circuit Analysis


%Simulate the circuit response for 1s in 1000 steps for a step function, a %sine function and a gaussian pulse.

```
C=0.25;
G1 = 1;
G2 = 1/2;
G3 = 1/8.5;
G4 = 1/0.1;
G0 = 1/1000;
L = 0.2;
alpha = 100;
```

```
% C and G Matrix
%F = V1, V2, V3, V4, V5, Vin, I4, IL
```

```
CVec = [-C, C, 0, 0, 0, 0, 0, 0;
        C, -C, 0, 0, 0, 0, 0, 0;
        0, 0, 0, 0, 0, 0, 0, 0;
        0, 0, 0, 0, 0, 0, 0, 0;
        0, 0, 0, 0, 0, 0, 0, 0;
        0, 0, 0, 0, 0, 0, 0, 0;
        0, 0, 0, 0, 0, 0, 0, 0;
        0, 0, 0, 0, 0, 0, -L, 0];
```

```
GVec = [-G1, G1, 0, 0, 0, -1, 0, 0;  
        G1, -G1-G2, 0, 0, 0, 0, 0, -1;  
        0, 0, -G3, 0, 0, 0, 0, 1;  
        0, 0, 0, -G4, G4, 0, 1, 0;  
        0, 0, 0, G4, -G4-G0, 0, 0, 0;  
        1, 0, 0, 0, 0, 0, 0, 0;  
        0, 0, -alpha*G3, 1, 0, 0, 0, 0;  
        0, 1, -1, 0, 0, 0, 0, 0];  
  
FVec = [0;0;0;0;0;1;0;0];  
  
vin = linspace(-10,10);  
outputV = zeros(size(vin));  
freq = linspace(0.01, 100);  
  
for a = 1:size(freq,2)  
    w = (2*pi*freq(a));  
    jw = 1i*w; % 1i makes value complex 1 -> 0+1j  
    V = (GVec+jw*CVec)\FVec;  
    outputV(a) = V(5);  
end  
  
%Plot Gain  
figure('Name','Circuit Frequency Response');  
semilogx(freq, 20*log(abs(outputV)));  
title('Frequency Response');  
xlabel('Frequency (Hz)');  
ylabel('Gain (dB)');  
  
% Question 4a) By inspection of the frequency response of the circuit, the  
% result is a low pass filter with the cut off frequency being around 2Hz.  
  
%Question 4b) The circuit has 40-46dB of gain for near DC values (any  
%frequency less than 2Hz). There is a slight slope for the gain so it is  
%not ideal.  
  
%Question 4c)  
%  $C(dV/dt) + GV = F$   
%  $C[(V_n - V_{n-1})/\delta_t] + G V_n = F(t_n)$   
%  $C(V_n/\delta_t) - C(V_{n-1}/\delta_t) + G V_n = F(t_n)$   
%  $V_n = [C(V_{n-1}/\delta_t) + F(t_n)] / (V_n/\delta_t)$ 
```

 

## Q4d - Step Response


```


t = 0:0.001:1; %Time 1000 steps 0 to 1
F1 = [0;0;0;0;0;0;0;0;0;0]; % initial values
vout = zeros(size(GVec,1),size(t,2)); % output vector
vin= zeros(1,size(t,2)); % input vector
vin(1,1) = 0; %initial input value

%Loop through time
for n=1:size(t,2)-1
    vout(:,n) = F1;
    if n<30 %Produce pulse
        vin(n+1)=0;
    else
        vin(n+1)=1;
    end
    F2 = FVec * vin(n+1); % Capturing next input
    F1 = ((CVec./0.001) + GVec)\((CVec./0.001)*F1 + F2);
end
vout(:,n+1) = F1;

figure("Name", "Step Response")
plot(t, vin, 'r');
hold on
plot(t, vout(5,:), 'b');
```
 
```
title('Step Response');  
xlabel('Time (s)');  
ylabel('Voltage (V)');  
legend({'Input', 'Output'});  
  
figure("Name", "Step Fourier Response Spectrum")  
semilogy(abs(fftshift(fft(vout(5,:)))))  
title('Step Fourier Response Spectrum');  
xlabel('Frequency (Hz)');  
ylabel('Magnitude');  
xlim([250 750]);
```



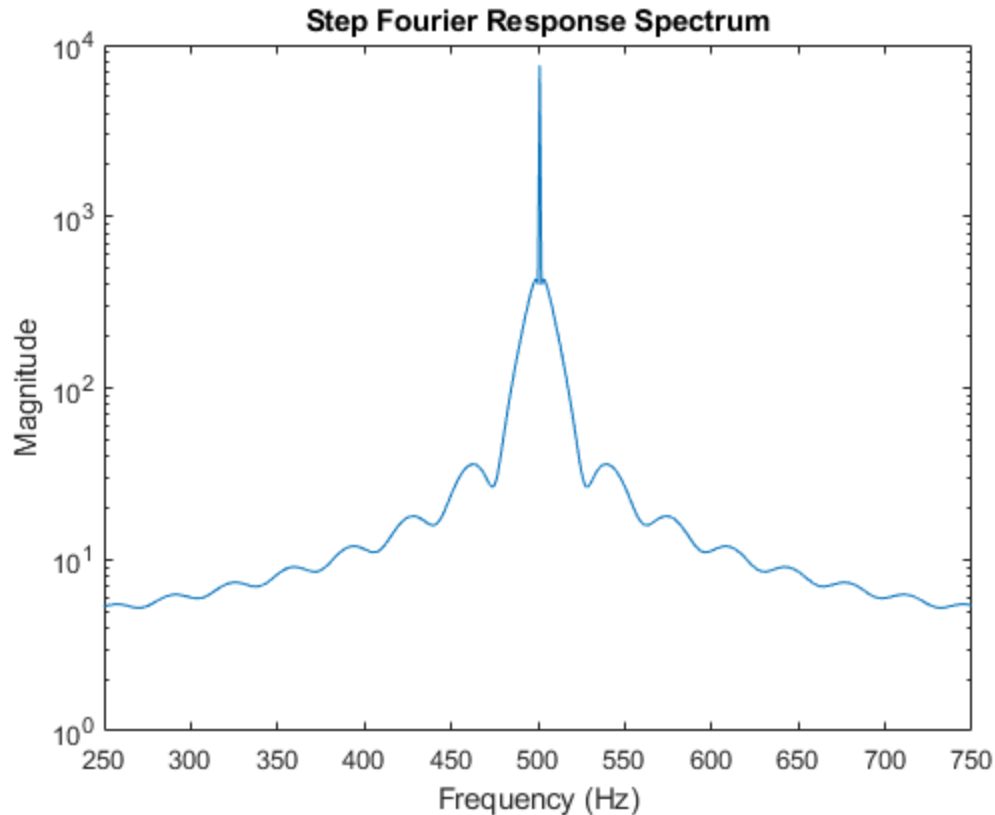

## Q4d - Step Response increasing time step

```

t = 0:0.002:1; %Time 1000 steps 0 to 1
F1 = [0;0;0;0;0;0;0;0;0;0]; % initial values
vout = zeros(size(GVec,1),size(t,2)); % output vector
vin= zeros(1,size(t,2)); % input vector
vin(1,1) = 0; %initial input value


%Loop through time
for n=1:size(t,2)-1
    vout(:,n) = F1;
    if n<30 %Produce pulse
        vin(n+1)=0;
    else
        vin(n+1)=1;
    end
    F2 = FVec * vin(n+1); % Capturing next input
    F1 = ((CVec./0.002) + GVec)\((CVec./0.002)*F1 + F2);
end
vout(:,n+1) = F1;


figure("Name","Step Response - Double Time Step")
plot(t, vin,'r');
hold on
plot(t, vout(5,:), 'b');
```

```
title('Step Response - Double Time Step');
xlabel('Time (s)');
ylabel('Voltage (V)');
legend({'Input', 'Output'});

figure("Name", "Step Fourier Response Spectrum - Larger Time Step")
semilogy(abs(fftshift(fft(vout(5,:)))))
title('Step Fourier Response Spectrum - Larger Time Step');
xlabel('Frequency (Hz)');
ylabel('Magnitude');
xlim([0 500])

 % When the time step doubles, the reaction time of the circuit is half and
% the base frequency is half as well for the step response (250Hz).
```



 

## Q4d - Sine wave @ Differnt frequency

```

t = 0:0.001:1;
freq2 = 1/0.03; % Frequency 33Hz
F1 = [0;0;0;0;0;0;0;0;0;0]; % initial values
vout2 = zeros(size(GVec,1),size(t,2)); % Vector to hold outputs
vin2 = zeros(1,size(t,2)); % Vector to hold inputs
vin2(1,1) = sin(2*pi*freq2*t(1));

%Loop through time
for n=1:size(t,2)-1
    vout2(:,n) = F1;
    vin2(1,n+1) = sin(2*pi*freq2*t(n+1));
    F2 = FVec * vin2(1,n+1);
    F1 = ((CVec./0.001) + GVec)\((CVec./0.001)*F1 + F2);
end
vout2(:,n+1) = F1;

figure("Name","Sine Wave Response 33Hz")
plot(t, vin2,'r');
hold on
plot(t, vout2(5,:), 'b');
title('Sine Wave Response 33Hz');
xlabel('Time (s)');
ylabel('Voltage (V)');

```



```
legend({'Input','Output'});

figure('Name','Sine Wave Fourier Response Spectrum 33Hz')
semilogy(abs(fftshift(fft(vout2(5,:))))))
title('Sine Wave Fourier Response Spectrum 33Hz');
xlabel('Frequency (Hz)');
ylabel('Magnitude');
xlim([250 750])

t = 0:0.001:1;
freq2 = 1; % Frequency in 1Hz
F1 = [0;0;0;0;0;0;0;0;0]; % initial values
vout2 = zeros(size(GVec,1),size(t,2)); % Vector to hold outputs
vin2 = zeros(1,size(t,2)); % Vector to hold inputs
vin2(1,1) = sin(2*pi*freq2*t(1));

%Loop through time
for n=1:size(t,2)-1
    vout2(:,n) = F1;
    vin2(1,n+1) = sin(2*pi*freq2*t(n+1));
    F2 = FVec * vin2(1,n+1);
    F1 = ((CVec./0.001) + GVec)\((CVec./0.001)*F1 + F2);
end
vout2(:,n+1) = F1;

figure('Name','Sine Wave Response 1Hz')
plot(t, vin2,'r');
hold on
plot(t, vout2(5,:), 'b');
title('Sine Wave Response');
xlabel('Time (s)');
ylabel('Voltage (V)');
legend({'Input','Output'});

figure('Name','Sine Wave Fourier Response Spectrum 1Hz')
semilogy(abs(fftshift(fft(vout2(5,:))))))
title('Sine Wave Fourier Response Spectrum 1Hz');
xlabel('Frequency (Hz)');
ylabel('Magnitude');
xlim([250 750])

freq2 = 1/0.01; % Frequency in 100Hz
F1 = [0;0;0;0;0;0;0;0;0]; % initial values
vout2 = zeros(size(GVec,1),size(t,2)); % Vector to hold outputs
vin2 = zeros(1,size(t,2)); % Vector to hold inputs
vin2(1,1) = sin(2*pi*freq2*t(1));

%Loop through time
for n=1:size(t,2)-1
    vout2(:,n) = F1;
    vin2(1,n+1) = sin(2*pi*freq2*t(n+1));
    F2 = FVec * vin2(1,n+1);
    F1 = ((CVec./0.001) + GVec)\((CVec./0.001)*F1 + F2);
end
```

```


vout2(:,n+1) = F1;



figure("Name","Sine Wave Response 100Hz")
plot(t, vin2,'r');
hold on
plot(t, vout2(5,:), 'b');
title('Sine Wave Response');
xlabel('Time (s)');
ylabel('Voltage (V)');
legend({'Input', 'Output'});



figure("Name","Sine Wave Fourier Response Spectrum 100Hz")
semilogy(abs(fftshift(fft(vout2(5,:))))))
title('Sine Wave Fourier Response Spectrum 100Hz');
xlabel('Frequency (Hz)');
ylabel('Magnitude');
xlim([250 750])


% Since the circuit is a low pass amplifier filter, the Gain of the circuit
% is optimal at the cutoff frequency. The 33Hz case had a gain of about
% double. increasing the frequency to 100Hz reduces the output gain to a
% decimal value so the output is smaller than the input. Any higher and
% therer would be no ouput as the signal would be completely blocked. Any
% case below the cutoff frequency would achive the maximum gain of the
% circuit.

```

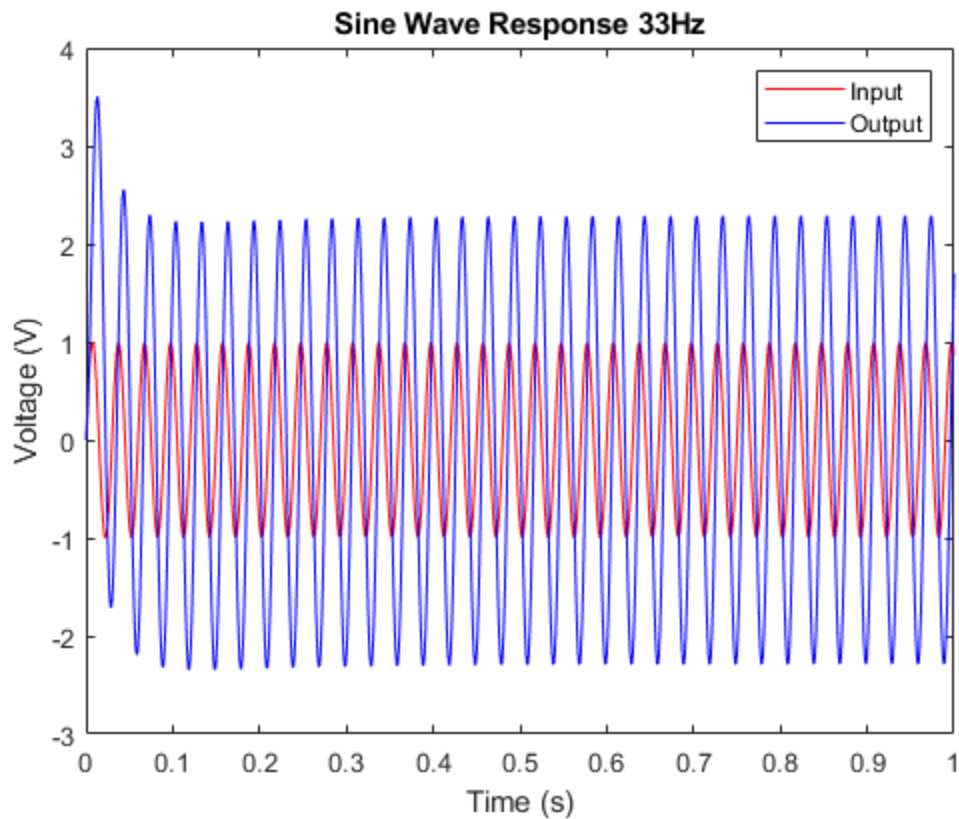

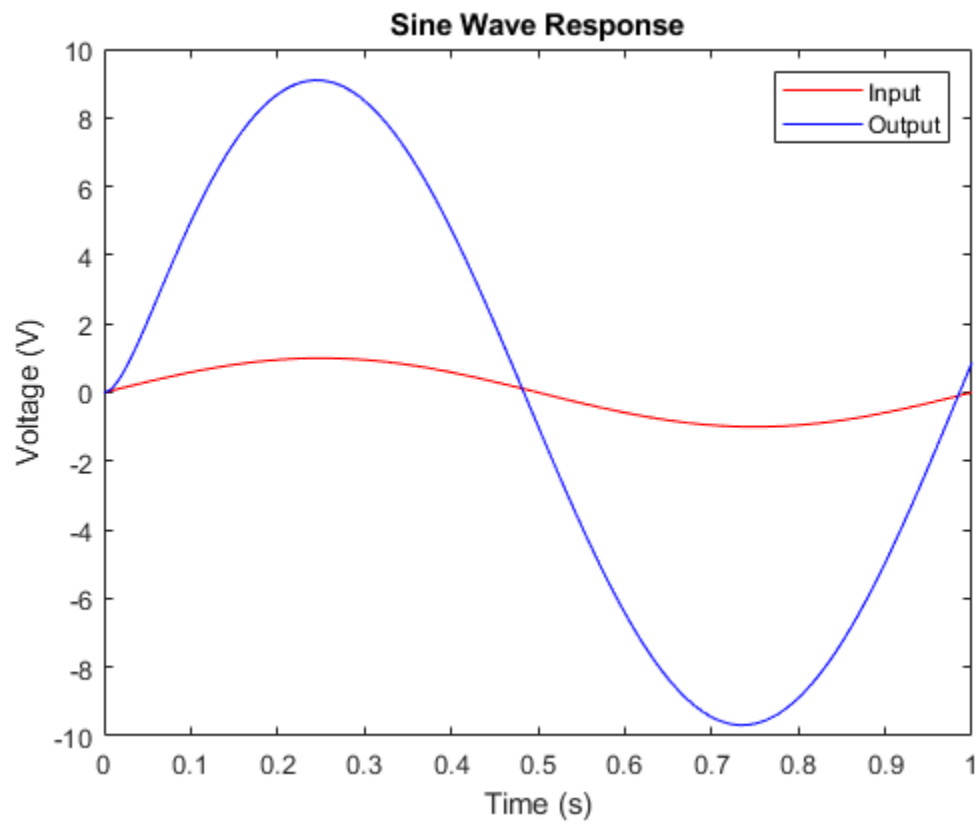 

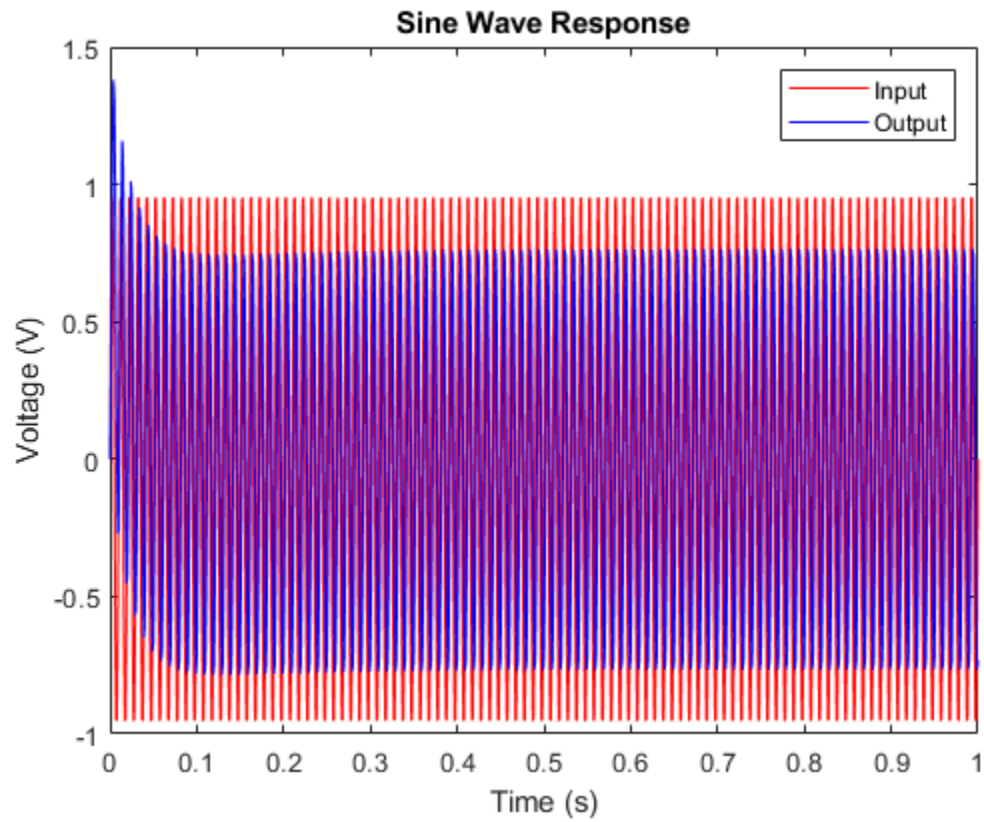 

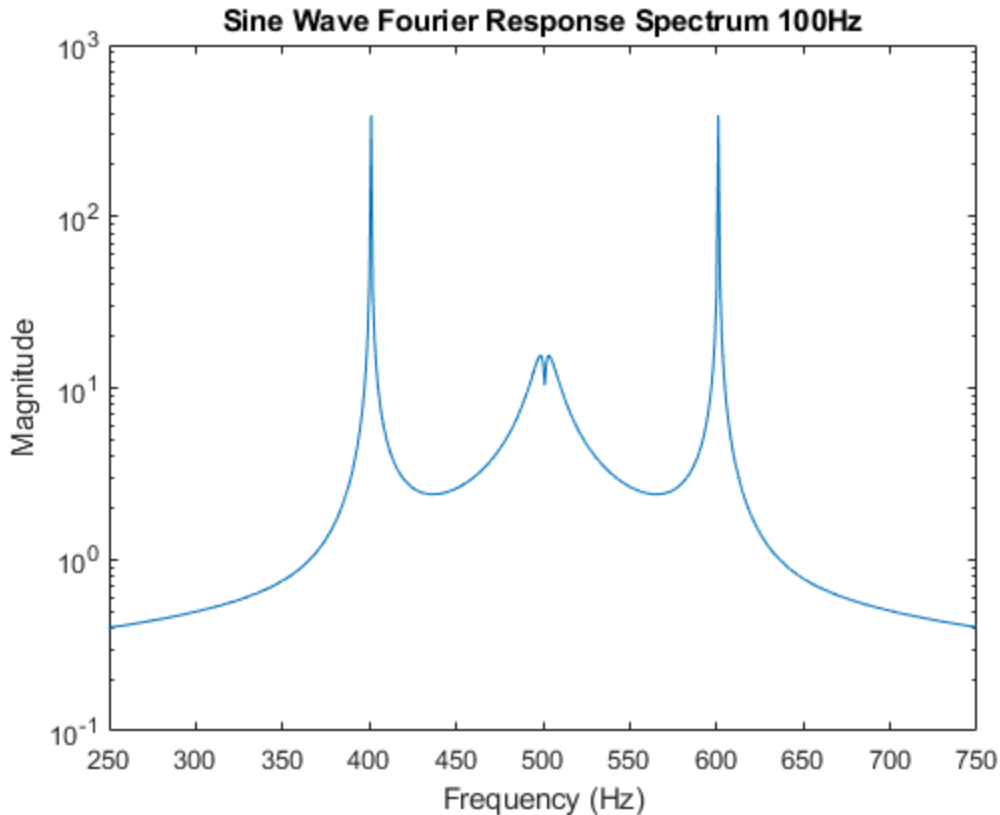

## Q4d - Sine wave @ Different frequency increasing time step

```

t = 0:0.002:1;
freq2 = 1/0.03; % Frequency 33Hz
F1 = [0;0;0;0;0;0;0;0;0;0]; % initial values
vout2 = zeros(size(GVec,1),size(t,2)); % Vector to hold outputs
vin2 = zeros(1,size(t,2)); % Vector to hold inputs
vin2(1,1) = sin(2*pi*freq2*t(1));

%Loop through time
for n=1:size(t,2)-1
    vout2(:,n) = F1;
    vin2(1,n+1) = sin(2*pi*freq2*t(n+1));
    F2 = FVec * vin2(1,n+1);
    F1 = ((CVec./0.002) + GVec)\((CVec./0.002)*F1 + F2);
end
vout2(:,n+1) = F1;


figure("Name","Sine Wave Response 33Hz - Double Time Step")
plot(t, vin2,'r');
hold on
plot(t, vout2(5,:), 'b');
title('Sine Wave Response 33Hz - Double Time Step');


```

```
xlabel('Time (s)');  
ylabel('Voltage (V)');  
legend({'Input','Output'});
```

```
figure('Name','Sine Wave Fourier Response Spectrum 33Hz')  
semilogy(abs(fftshift(fft(vout2(5,:))))))  
xlabel('Frequency (Hz)');  
title('Sine Wave Fourier Response Spectrum 33Hz');  
ylabel('Magnitude');  
xlim([0 500])
```

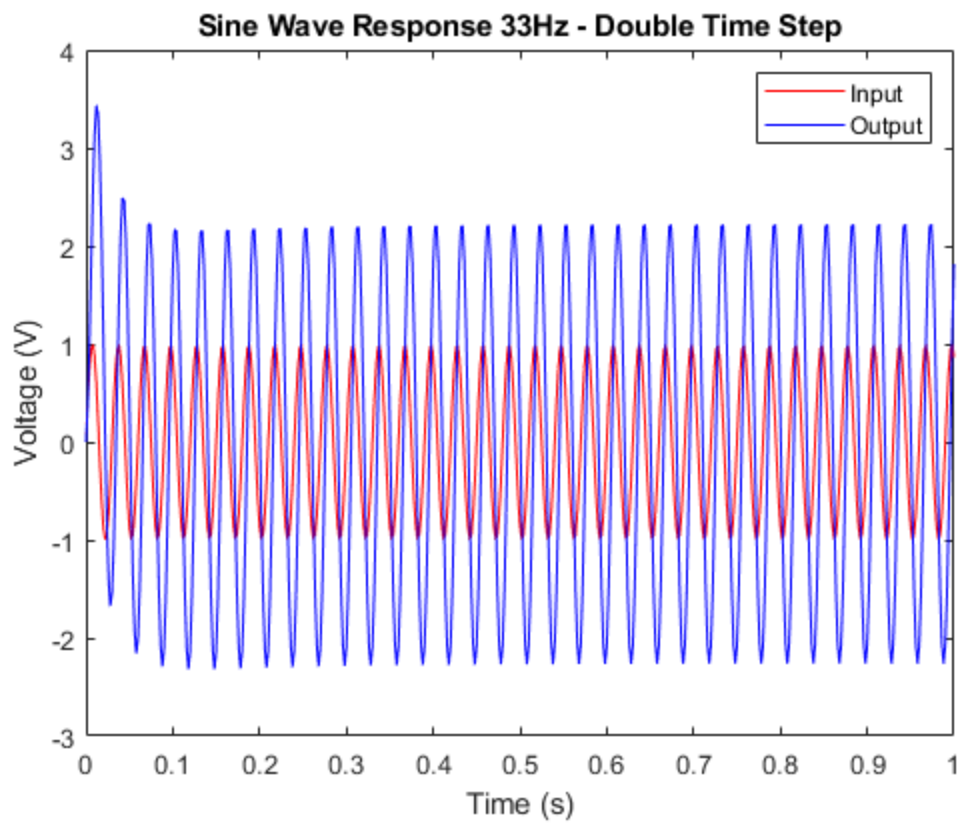% When the time step doubles, the reaction time of the circuit is half and  
% the base frequency is half as well for the AC response (250Hz base).



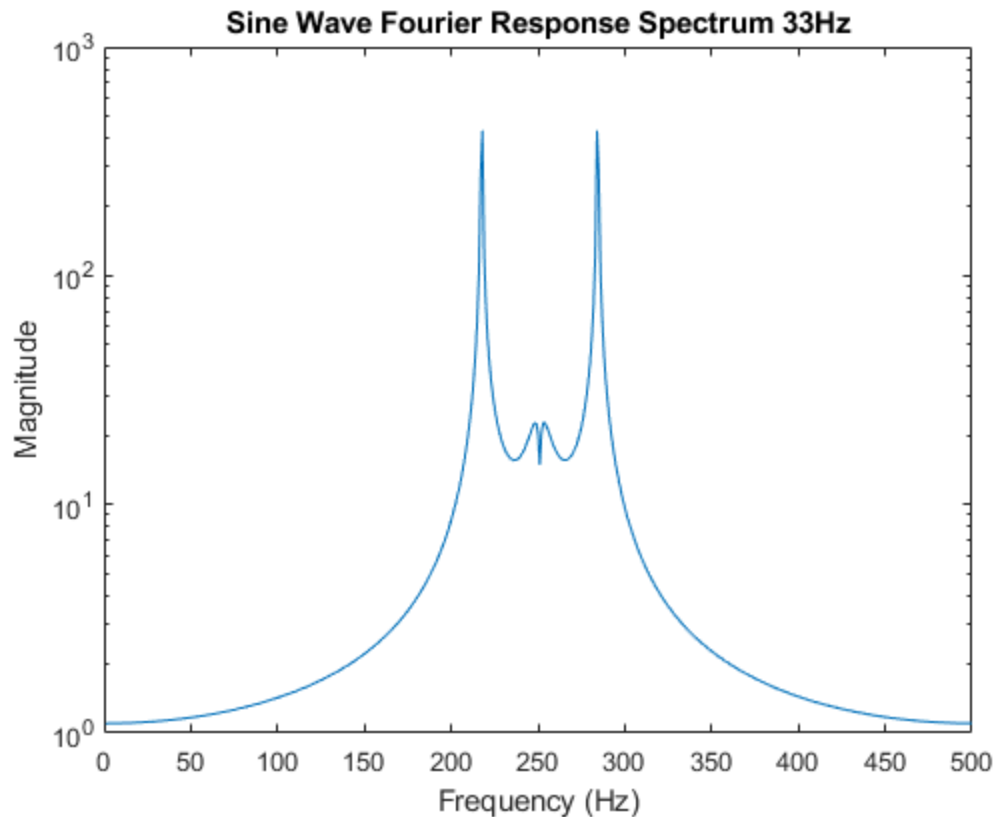

## Q4d - Gaussian Pulse Response

```

F1 = [0;0;0;0;0;0;0;0;0;0]; % initial values
vout3 = zeros(size(GVec,1),size(t,2)); % Vector to hold outputs
vin3 = zeros(1,size(t,2)); % Vector to hold inputs

t = 0:0.001:1;


%https://www.gaussianwaves.com/2014/07/generating-basic-signals-gaussian-
pulse-and-power-spectral-density-using-fft/
std = 0.03;
delay = 0.06^2;
vin3(1,1) = 1/(sqrt(2*pi*delay))*(exp(-t(1).^2/(2*delay)));

for n=1:size(t,2)-1
    vout3(:,n) = F1;
    vin3(1,n+1) = 1/(sqrt(2*pi*delay))*(exp(-t(n+1).^2/(2*delay)));
    F2 = FVec * vin3(1,n+1);
    F1 = ((CVec./0.001) + GVec)\((CVec./0.001)*F1 + F2);
end
vout3(:,n+1) = F1;


figure("Name","Gaussian Pulse Response")
plot(t, vin3,'r');
hold on

```
 
```
plot(t, vout3(5,:), 'b');  
title('Gaussian Pulse Response');  
xlabel('Time (s)');  
ylabel('Voltage (V)');  
legend({'Input', 'Output'});  
  
figure("Name", "Gaussian Pulse Fourier Response Spectrum")  
semilogy(abs(fftshift(fft(vout3(5,:)))))  
title('Gaussian Pulse Fourier Response');  
xlabel('Frequency (Hz)');  
ylabel('Magnitude');  
xlim([250 750])
```





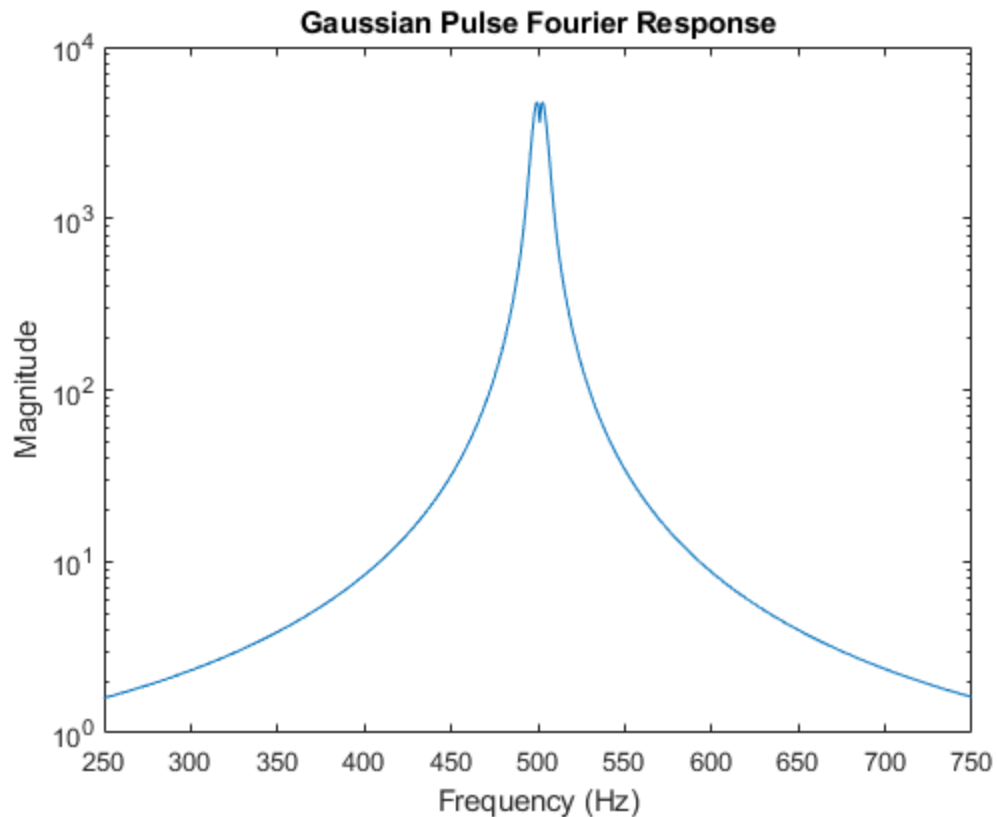

## Question 5 - Introduction of circuit noise

```

C=0.25;
Cn = 0.00001;
G1 = 1;
G2 = 1/2;
G3 = 1/8.5;
G4 = 1/0.1;
G0 = 1/1000;
L = 0.2;
alpha = 100;

%F = V1, V2, V3, V4, V5, Vin, I4, IL


% 0 = Iin - G1(V1-V2) - C*d(V1-V2)/dt
% 0 = G1(V1-V2) + C*d(V1-V2)/dt - V2*G2 - IL
% 0 = IL - G3*V3 - V3*Cn + In
% 0 = I4 - G4*(V4-V5)
% 0 = G4*(V4-V5) - Go*Vo
% Vin = V1
% V4 = I3*Alpha = -Alpha*G3*V3
% dIL = dt(V2-V3)/L



% Updated C Matrix

```

```
CVec = [-C, C, 0, 0, 0, 0, 0, 0, 0;  
        C, -C, 0, 0, 0, 0, 0, 0, 0;  
        0, 0, Cn, 0, 0, 0, 0, 0, 0;  
        0, 0, 0, 0, 0, 0, 0, 0, 0;  
        0, 0, 0, 0, 0, 0, 0, 0, 0;  
        0, 0, 0, 0, 0, 0, 0, 0, 0;  
        0, 0, -alpha*Cn, 0, 0, 0, 0, 0, 0;  
        0, 0, 0, 0, 0, 0, 0, 0, -L];  
  
GVec = [-G1, G1, 0, 0, 0, -1, 0, 0, 0;  
        G1, -G1-G2, 0, 0, 0, 0, 0, 0, -1;  
        0, 0, -G3, 0, 0, 0, 0, 0, 1;  
        0, 0, 0, -G4, G4, 0, 1, 0, 0;  
        0, 0, 0, G4, -G4-G0, 0, 0, 0, 0;  
        1, 0, 0, 0, 0, 0, 0, 0, 0;  
        0, 0, -alpha*G3, 1, 0, 0, 0, 0, 0;  
        0, 1, -1, 0, 0, 0, 0, 0, 0];  
  
FVec = [0;0;1;0;0;1;0;0]; %Include new current source for R3  
  
t = 0:0.001:1;  
F1 = [0;0;0;0;0;0;0;0;0];  
In = 0.001*randn(1,size(t,2));  
vout = zeros(size(GVec,1),size(t,2));  
vin= zeros(1,size(t,2));  
vin(1,1) = In(1);  
  
std = 0.03;  
delay = 0.06^2;  
vin(1,1) = 1/(sqrt(2*pi*delay))*(exp(-t(1).^2/(2*delay)));  
  
for n=1:size(t,2)-1  
    vout(:,n) = F1;  
    vin(1,n+1) = 1/(sqrt(2*pi*delay))*(exp(-t(n+1).^2/(2*delay)));  
    F2 = FVec * In(n+1); %Add noise to node 3  
    F2(6) = vin(n+1); %Add input  
    F1 = ((CVec./0.001) + GVec)\((CVec./0.001)*F1 + F2);  
end  
vout(:,n+1) = F1;  
  
figure("Name","Current Noise Histogram")  
histogram(In);  
xlabel('Noise Current (A)');  
ylabel('Number in Bin (#)');  
title('Noise Histogram');  
  
figure("Name","Gaussian Pulse Response")  
plot(t, vin,'r');  
hold on  
plot(t, vout(5,:), 'b');  
title('Gaussian Pulse Response');  
xlabel('Time (s)');
```
 
```
ylabel('Voltage (V)');  
legend({'Input', 'Output'});  
  
figure('Name', 'Gaussian Pulse Fourier Response Spectrum')  
semilogy(abs(fftshift(fft(vout(5,:))))))  
title('Gaussian Pulse Fourier Response');  
xlabel('Frequency (Hz)');  
ylabel('Magnitude');  
xlim([250 750])
```



  

## Q5 Changing Cn

```

t = 0:0.001:1;
F1 = [0;0;0;0;0;0;0;0;0];
In = 0.001*randn(1,size(t,2));
vout = zeros(size(GVec,1),size(t,2));
vin= zeros(1,size(t,2));
vin(1,1) = In(1);

std = 0.03;
delay = 0.06^2;
vin(1,1) = 1/(sqrt(2*pi*delay))*(exp(-t(1).^2/(2*delay)));

a = linspace(0.000005, 0.00005,4);

for x = 1:size(a,2)
    Cn = a(x);

    CVec = [-C, C, 0, 0, 0, 0, 0, 0, 0;
            C, -C, 0, 0, 0, 0, 0, 0, 0;
            0, 0, Cn, 0, 0, 0, 0, 0, 0;
            0, 0, 0, 0, 0, 0, 0, 0, 0;
            0, 0, 0, 0, 0, 0, 0, 0, 0;
            0, 0, 0, 0, 0, 0, 0, 0, 0;
            0, 0, -alpha*Cn, 0, 0, 0, 0, 0, 0;
            0, 0, 0, 0, 0, 0, 0, 0, -L;];


    for n=1:size(t,2)-1
        vout(:,n) = F1;
        vin(1,n+1) = 1/(sqrt(2*pi*delay))*(exp(-t(n+1).^2/(2*delay)));
        F2 = FVec * In(n+1); %Add noise to node 3
        F2(6) = vin(n+1); %Add input
        F1 = ((CVec./0.001) + GVec)\((CVec./0.001)*F1 + F2);
    end
    vout(:,n+1) = F1;



    figure("Name","Gaussian Pulse Response ")
    plot(t, vin,'r');
    hold on
    plot(t, vout(5,:), 'b');
    title('Gaussian Pulse Response, Capacitance(F) = ',Cn);
    xlabel('Time (s)');
    ylabel('Voltage (V)');
    legend({'Input','Output'});



    figure("Name","Gaussian Pulse Fourier Response Spectrum")
    semilogy(abs(fftshift(fft(vout(5,:)))));
    title('Gaussian Pulse Fourier Response');
    xlabel('Frequency (Hz)');
    ylabel('Magnitude');
    xlim([250 750]);
end

```


 
% Increasing the value of the capacitor changes the effect of the noise on  
% the circuit, the value cannot be increased too much or else the circuit  
% fails.




  

  



  

 

## Q5 Changing Time Step

```

C=0.25;
Cn = 0.00001;
G1 = 1;
G2 = 1/2;
G3 = 1/8.5;
G4 = 1/0.1;
G0 = 1/1000;
L = 0.2;
alpha = 100;

CVec = [-C, C, 0, 0, 0, 0, 0, 0, 0;
        C, -C, 0, 0, 0, 0, 0, 0, 0;
        0, 0, Cn, 0, 0, 0, 0, 0, 0;
        0, 0, 0, 0, 0, 0, 0, 0, 0;
        0, 0, 0, 0, 0, 0, 0, 0, 0;
        0, 0, 0, 0, 0, 0, 0, 0, 0;
        0, 0, -alpha*Cn, 0, 0, 0, 0, 0, 0;
        0, 0, 0, 0, 0, 0, 0, 0, -L];

GVec = [-G1, G1, 0, 0, 0, -1, 0, 0, 0;
        G1, -G1-G2, 0, 0, 0, 0, 0, 0, -1;
        0, 0, -G3, 0, 0, 0, 0, 0, 1;
        0, 0, 0, -G4, G4, 0, 0, 1, 0];

```

```
0, 0, 0, G4, -G4-G0, 0, 0, 0;
1, 0, 0, 0, 0, 0, 0, 0;
0, 0, -alpha*G3, 1, 0, 0, 0, 0;
0, 1, -1, 0, 0, 0, 0, 0];

FVec = [0;0;1;0;0;1;0;0]; %Include new current source for R3

t = 0:0.002:1;
F1 = [0;0;0;0;0;0;0;0];
In = 0.002*randn(1,size(t,2));
vout = zeros(size(GVec,1),size(t,2));
vin= zeros(1,size(t,2));
vin(1,1) = In(1);

std = 0.03;
delay = 0.06^2;
vin(1,1) = 1/(sqrt(2*pi*delay))*(exp(-t(1).^2/(2*delay)));

for n=1:size(t,2)-1
    vout(:,n) = F1;
    vin(1,n+1) = 1/(sqrt(2*pi*delay))*(exp(-t(n+1).^2/(2*delay)));
    F2 = FVec * In(n+1); %Add noise to node 3
    F2(6) = vin(n+1); %Add input
    F1 = ((CVec./0.002) + GVec)\((CVec./0.002)*F1 + F2);
end
vout(:,n+1) = F1;

figure("Name","Gaussian Pulse Response - Time Step = 0.002")
plot(t, vin,'r');
hold on
plot(t, vout(5,:), 'b');
title('Gaussian Pulse Response- Time Step = 0.002');
xlabel('Time (s)');
ylabel('Voltage (V)');
legend({'Input', 'Output'});

figure("Name","Gaussian Pulse Fourier Response Spectrum")
semilogy(abs(fftshift(fft(vout(5,:)))))
title('Gaussian Pulse Fourier Response- Time Step = 0.002');
xlabel('Frequency (Hz)');
ylabel('Magnitude');
xlim([0 500]);

t = 0:0.0005:1;
F1 = [0;0;0;0;0;0;0;0];
In = 0.0005*randn(1,size(t,2));
vout = zeros(size(GVec,1),size(t,2));
vin= zeros(1,size(t,2));
vin(1,1) = In(1);

std = 0.03;
delay = 0.06^2;
vin(1,1) = 1/(sqrt(2*pi*delay))*(exp(-t(1).^2/(2*delay)));
```


```



for n=1:size(t,2)-1
    vout(:,n) = F1;
    vin(1,n+1) = 1/(sqrt(2*pi*delay))*(exp(-t(n+1).^2/(2*delay)));
    F2 = FVec * In(n+1); %Add noise to node 3
    F2(6) = vin(n+1); %Add input
    F1 = ((CVec./0.0005) + GVec)\((CVec./0.0005)*F1 + F2);
end
vout(:,n+1) = F1;


figure("Name","Gaussian Pulse Response - Time Step = 0.0005")
plot(t, vin, 'r');
hold on
plot(t, vout(5,:), 'b');
title('Gaussian Pulse Response- Time Step = 0.0005');
xlabel('Time (s)');
ylabel('Voltage (V)');
legend({'Input', 'Output'});

figure("Name","Gaussian Pulse Fourier Response Spectrum")
semilogy(abs(fftshift(fft(vout(5,:)))))
title('Gaussian Pulse Fourier Response- Time Step = 0.0005');
xlabel('Frequency (Hz)');
ylabel('Magnitude');
xlim([500 1500]);

```

 

  

 

*Published with MATLAB® R2021b*